

- 6 Fig. 6.1 shows part of a bridge rectifier circuit that can be used for rectification of an alternating input voltage V_{IN} .

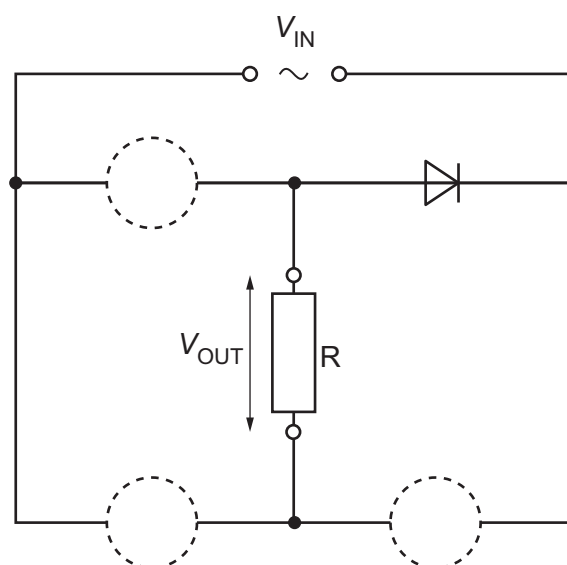


Fig. 6.1

The circuit contains four diodes, one of which is shown.
The rectified output voltage V_{OUT} is applied across load resistor R .

- (a) (i) State what is meant by rectification.

.....
..... [1]

- (ii) State the name of the type of rectification produced by a bridge rectifier circuit.

..... [1]

- (iii) Complete the circuit in Fig. 6.1 by drawing the three missing diodes inside the dashed circles. [2]

- (b) The input voltage varies with time t according to the equation

$$V_{IN} = 34 \sin 18t$$

where V_{IN} is in V and t is in s.

- (i) Show that the period of the input voltage is 0.35 s.

[2]

- (ii) Calculate the root-mean-square (r.m.s.) input voltage.

r.m.s. voltage = V [1]

- (iii) On Fig. 6.2, sketch the variation of V_{OUT} with t from $t = 0$ to $t = 0.35$ s.

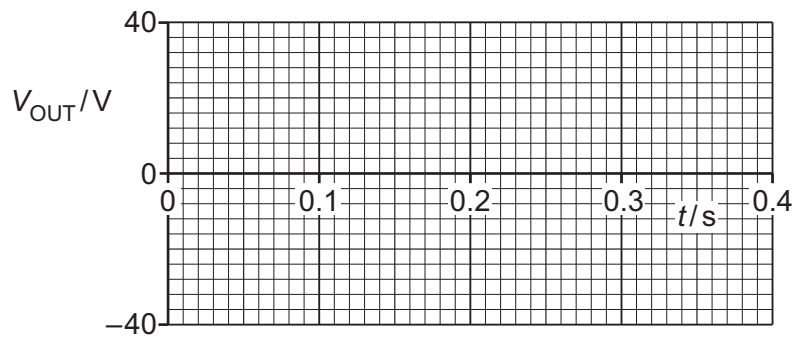


Fig. 6.2

[3]

- (c) Resistor R has a resistance of $56 \text{ k}\Omega$. A capacitor of capacitance $12 \mu\text{F}$ is connected into the circuit of Fig. 6.1 in order to smooth the output voltage.

- (i) On Fig. 6.1, draw the capacitor correctly connected into the circuit. [1]

- (ii) Calculate the time constant of the smoothing circuit.

time constant = s [2]

(iii) During each discharge cycle, the time for which the capacitor is discharging is 0.14 s.

Determine the minimum value of the smoothed output voltage.

minimum voltage = V [2]

- 7 An alternating voltage V varies with time t according to

$$V = 18 \cos 40\pi t$$

where V is in V and t is in s.

- (a) For the alternating voltage:

- (i) show that the period is 0.050 s

[1]

- (ii) determine the root-mean-square (r.m.s.) voltage.

r.m.s. voltage = V [1]

- (b) On Fig. 7.1, sketch the variation of V with t for values of t from $t = 0$ to $t = 100$ ms.

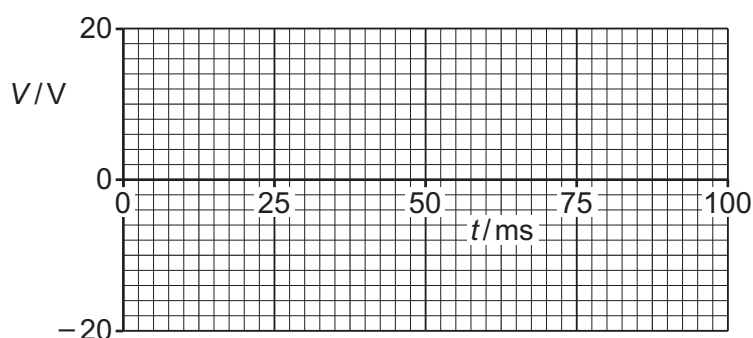


Fig. 7.1

[3]

- (c) The alternating voltage is rectified to produce an output voltage across a load resistor R , as shown in Fig. 7.2.

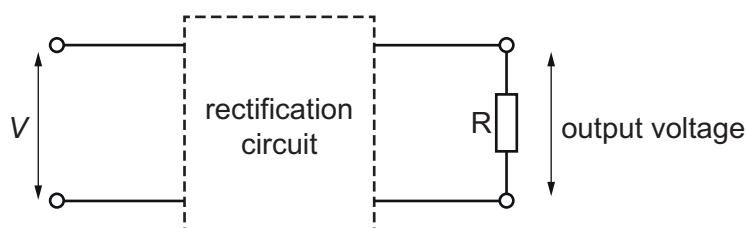


Fig. 7.2

Fig. 7.3 shows the variation with t of the power P in the load resistor.

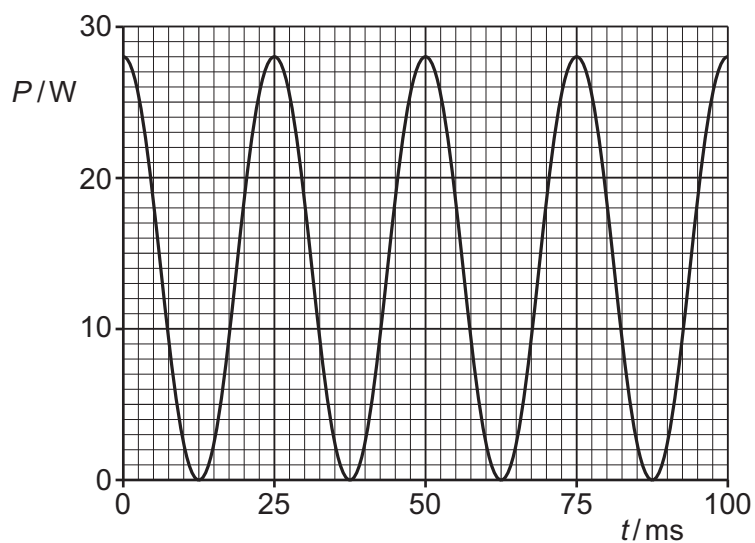


Fig. 7.3

State **three** conclusions that can be drawn from Fig. 7.3. The conclusions may be qualitative or quantitative. Use the space for any working.

1

.....

2

.....

3

.....

[3]

- 8 An incomplete circuit diagram of a bridge rectifier is shown in Fig. 8.1.

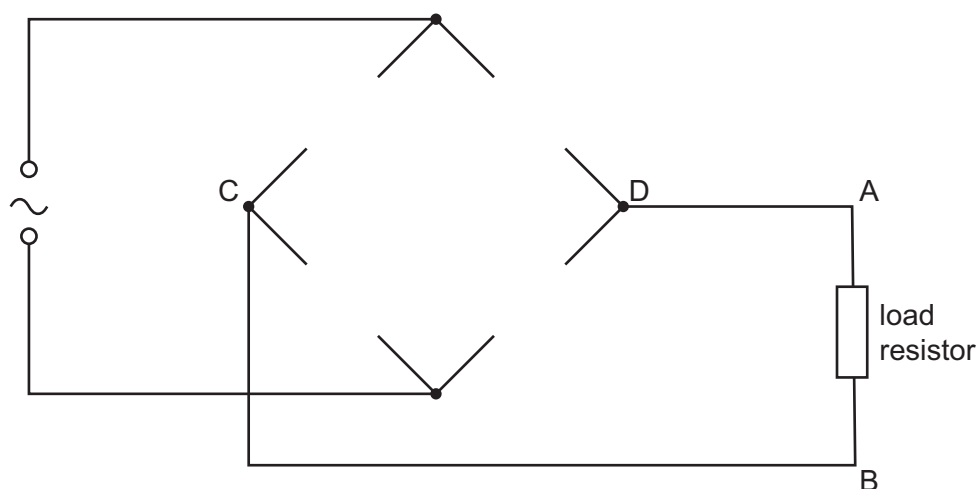


Fig. 8.1

- (a) Complete Fig. 8.1 for the bridge rectifier such that the point A is at a positive potential with respect to point B. [2]
- (b) The variation with time t of the potential difference (p.d.) V across the load resistor is shown in Fig. 8.2.

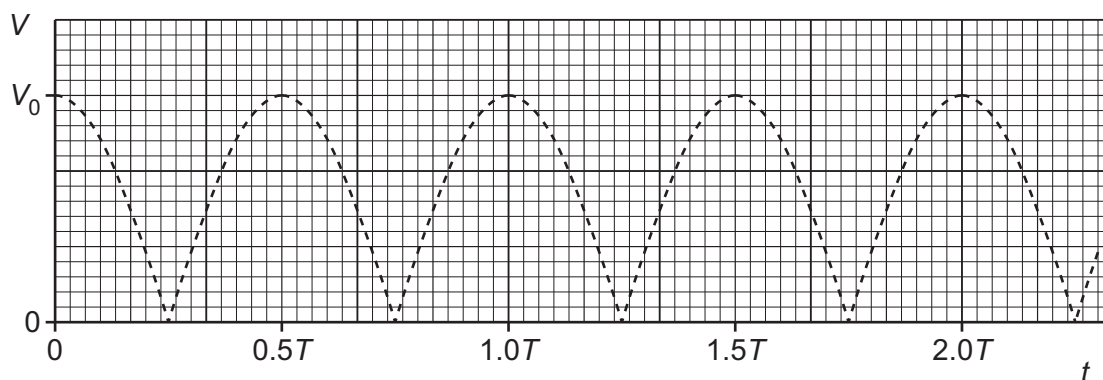


Fig. 8.2

A capacitor is now connected between points C and D of the bridge rectifier. This results in smoothing of the p.d. across the load resistor. The difference between the maximum and minimum values of the smoothed p.d. is 33% of the peak p.d. V_0 .

- (i) On Fig. 8.2, draw a line to show the variation of the potential difference V across the load resistor with time t . Your line should extend from $t = 0.5T$ to $t = 2.0T$. [3]

- (ii) Use your line in (b)(i) to determine, in terms of T , the time constant of the smoothing circuit.

time constant = T [3]

- (iii) The resistance of the load resistor is now increased. The capacitance of the capacitor is unchanged.

State and explain the effect of this change on the smoothed output p.d.

.....
.....
..... [2]

8 Fig. 8.1 shows a circuit that produces rectification of an alternating input voltage.

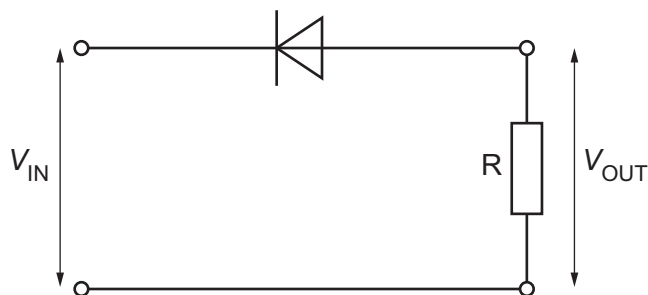


Fig. 8.1

The input voltage V_{IN} is sinusoidal. The rectified output voltage V_{OUT} is applied across resistor R .

The variation of V_{IN} with time t has amplitude V_0 and period T , as shown in Fig. 8.2.

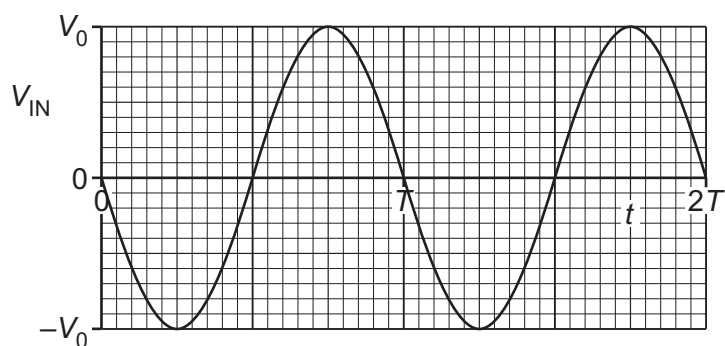


Fig. 8.2

The root-mean-square (r.m.s.) value of V_{IN} is 6.0 V.

(a) (i) State the type of rectification produced by the circuit of Fig. 8.1.

..... [1]

(ii) Calculate V_0 .

$V_0 =$ V [1]

(b) Resistor R has resistance 45Ω .

Assume that there is no p.d. across the diode when it is conducting.

(i) Determine the peak power P_0 in the resistor.

$P_0 = \dots\dots\dots$ W [2]

(ii) On Fig. 8.3, sketch the variation of the power P in the resistor with t between $t = 0$ and $t = 2T$.

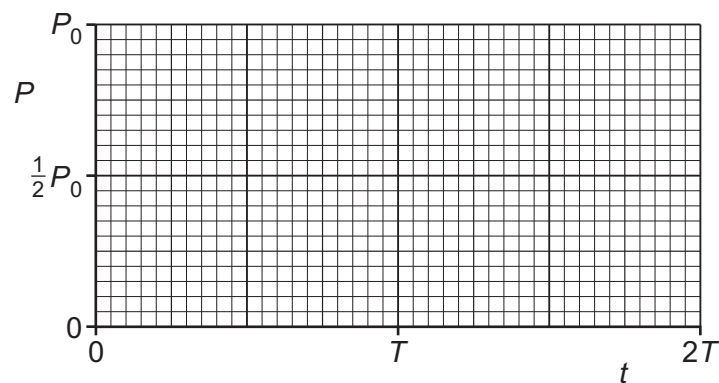


Fig. 8.3

[3]

(iii) Use the answer in (b)(ii) to explain why the mean power in the resistor is $\frac{1}{4}P_0$.

.....

 [2]

(iv) Use the information in (b)(iii) to determine the r.m.s. value of V_{OUT} .

r.m.s. voltage = V [1]

- 6 Fig. 6.1 shows a circuit that rectifies an alternating input voltage V_{IN} and produces an output voltage V_{OUT} across a resistor R .

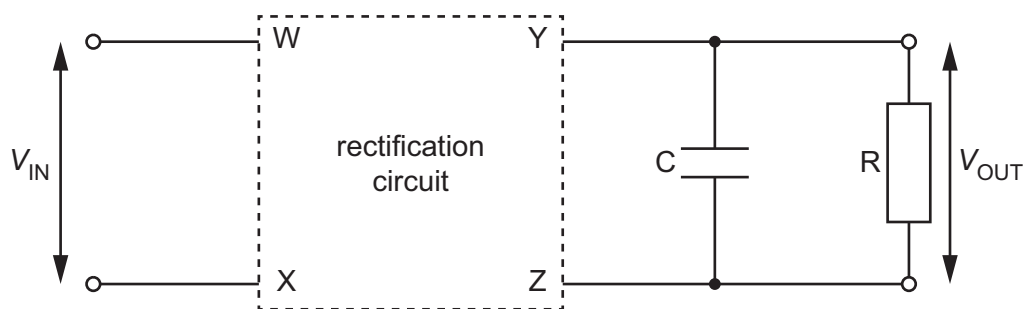


Fig. 6.1

The four terminals of the rectification circuit are labelled W, X, Y and Z.
A capacitor C is connected in parallel with resistor R .

- (a) (i) State what is meant by rectification.

.....
 [1]

- (ii) State the purpose of capacitor C .

.....
 [1]

- (b) Fig. 6.2 shows the variations with time t of the potential differences (p.d.s) V_{IN} and V_{OUT} .

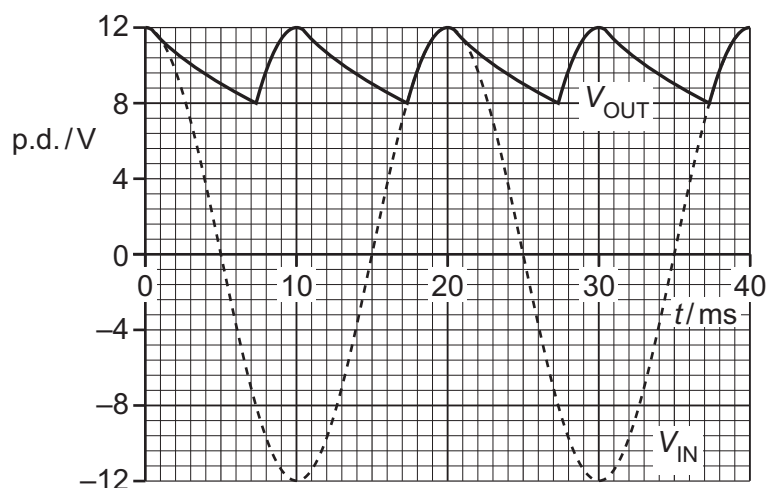


Fig. 6.2

- (i) The variation of V_{IN} with t can be represented by

$$V_{IN} = A \cos Bt$$

where A and B are constants.

Determine the values of A and B . Give a unit with your answer for A .

$A = \dots\dots\dots$ unit $\dots\dots\dots$

$B = \dots\dots\dots \text{rad s}^{-1}$
[2]

- (ii) Determine the type of rectification produced by the circuit in Fig. 6.1.

$\dots\dots\dots$ [1]

- (iii) On Fig. 6.3, draw the circuit diagram for the components inside the rectification circuit.



Fig. 6.3

[2]

- (iv) Determine a value for the time constant for the discharge of the capacitor C through the resistor R in Fig. 6.1.

time constant = $\dots\dots\dots$ s [3]

(c) The capacitor C has a capacitance of $570\text{ }\mu\text{F}$.

Use your answer in (b)(iv) to determine the resistance of resistor R.

resistance = Ω [2]



- 8 (a) State what is meant by the frequency of an alternating current.

.....
..... [1]

- (b) An alternating current I in a resistor of resistance $680\ \Omega$ varies with time t according to

$$I = 3.5 \sin(40\pi t)$$

where I is in A and t is in s.

- (i) Show that the period of the alternating current is 50 ms.

[1]

- (ii) On Fig. 8.1, sketch the variation of I with t between $t = 0$ and $t = 100$ ms.

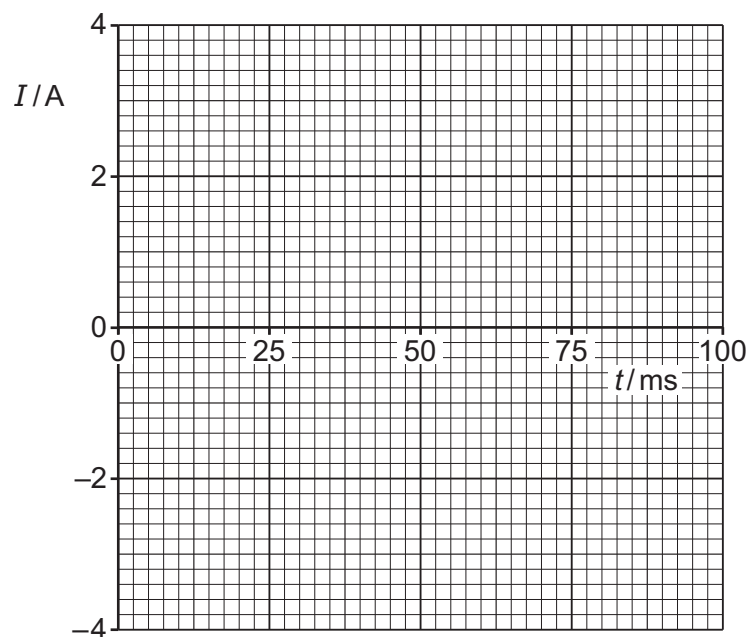


Fig. 8.1

[3]



(iii) Determine the root-mean-square (r.m.s.) current in the resistor.

r.m.s. current =A [1]

(c) Use data from (b), including your answer in (b)(iii), to show by calculation that the mean power in the 680Ω resistor is half of the peak power.

[3]



- 6 (a) (i) State what is meant by rectification of an alternating voltage.

.....
..... [1]

- (ii) State the difference between half-wave rectification and full-wave rectification.

.....
.....
..... [2]

- (b) (i) Complete Fig. 6.1 to show a circuit that produces half-wave rectification of an alternating input voltage V_{IN} to produce output voltage V_{OUT} across the resistor R .

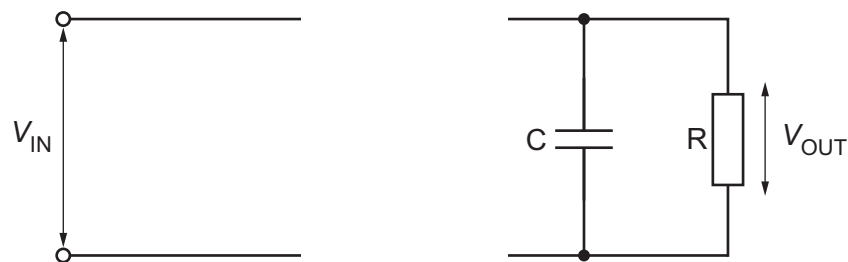


Fig. 6.1

[2]

- (ii) State the purpose of the capacitor C in the circuit of Fig. 6.1.

.....
..... [1]

- (c) The input voltage V_{IN} in Fig. 6.1 is a square wave. Fig. 6.2 shows the variation of V_{IN} with time t .

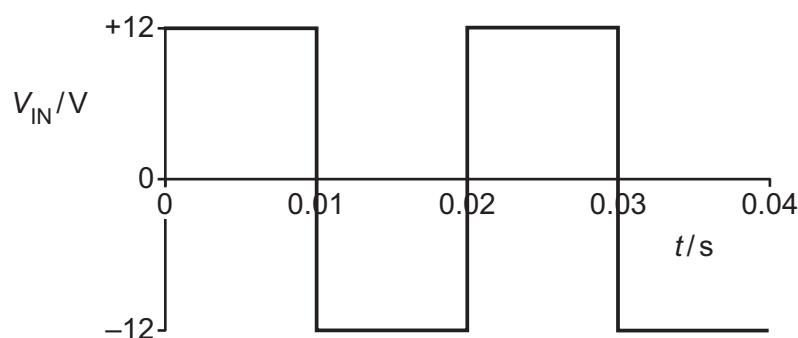


Fig. 6.2

Fig. 6.3 shows the variation of V_{OUT} with t .

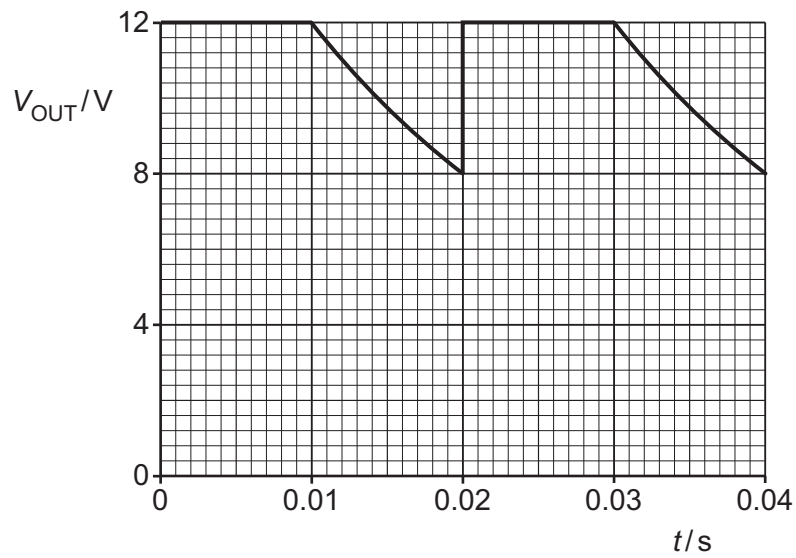


Fig. 6.3

The maximum energy stored in the capacitor is 0.041 J.

(i) Show that the capacitance of C is $570 \mu\text{F}$.

[2]

(ii) Determine the resistance of R .

resistance = Ω [3]

- 7 A circuit contains a power supply that provides a sinusoidal alternating input voltage V_{IN} . There is an output voltage V_{OUT} across a load resistor R , as shown in Fig. 7.1.

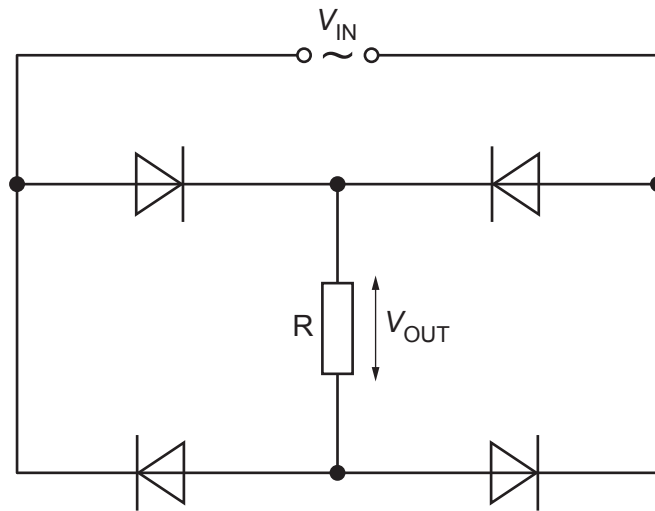


Fig. 7.1

- (a) State the purpose of the circuit in Fig. 7.1.

.....

.....

..... [2]

- (b) Fig. 7.2 shows the variation of V_{OUT} with time t .

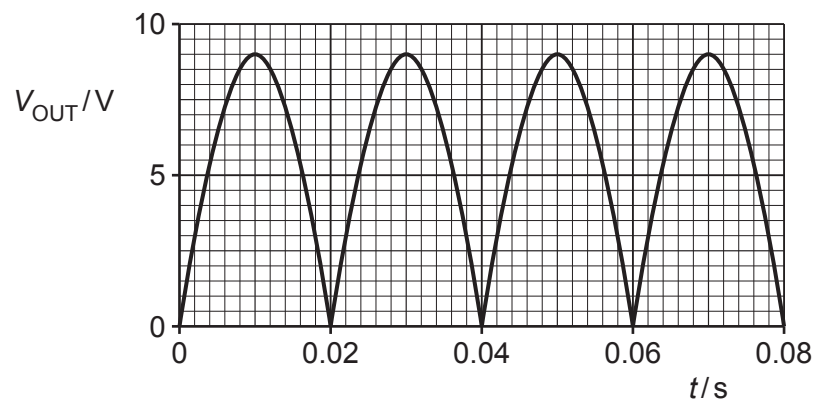


Fig. 7.2

- (i) The load resistor R has a resistance of $370\ \Omega$.

Show that the maximum power dissipated in R is 0.22 W .

[2]

- (ii) On Fig. 7.3, sketch the variation with t of the power P dissipated in R .

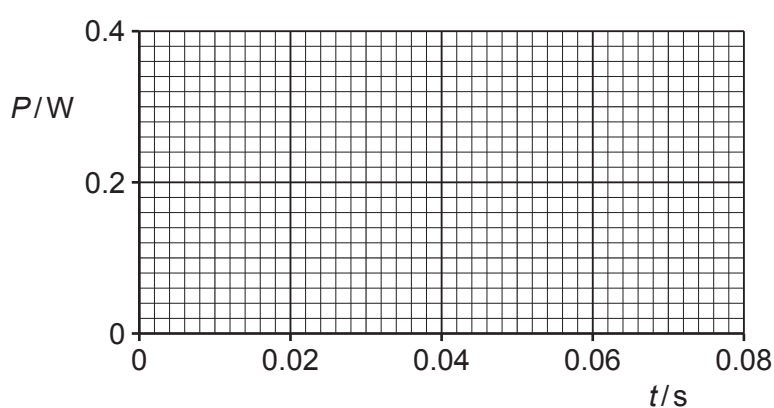


Fig. 7.3

[3]

- (iii) Calculate the mean power dissipated in R .

mean power = W [1]

- (c) The circuit of Fig. 7.1 is disconnected, and R is connected directly across the power supply.

Explain, without calculation, how the mean power now dissipated in R compares with the answer in (b)(iii).

.....

 [2]

- 4 (a) Three capacitors are connected as shown in Fig. 4.1.

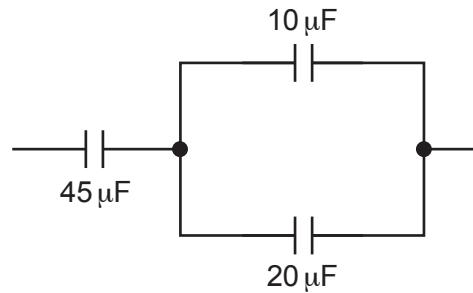


Fig. 4.1

Determine the total capacitance, in μF , of the network of three capacitors.

capacitance = μF [2]

- (b) A capacitor of capacitance $45\ \mu\text{F}$ is connected to a variable power supply initially set at $8.0\ \text{V}$. The output of the power supply increases so that the potential difference (p.d.) across the capacitor increases to $9.6\ \text{V}$.

Calculate the increase in energy ΔE stored in the capacitor.

$\Delta E = \dots\dots\dots\ \text{J}$ [2]

- (c) A sinusoidal a.c. power supply is connected to the input of a bridge rectifier. The output of the rectifier is connected to a load resistor.

- (i) Complete the circuit in Fig. 4.2 by adding a capacitor to smooth the p.d. across the load resistor.

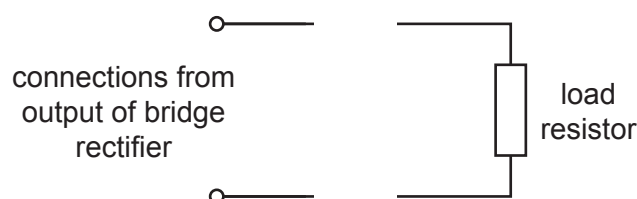


Fig. 4.2

[1]

(ii) The variation with time t of the p.d. V of the smoothed output is shown in Fig. 4.3.

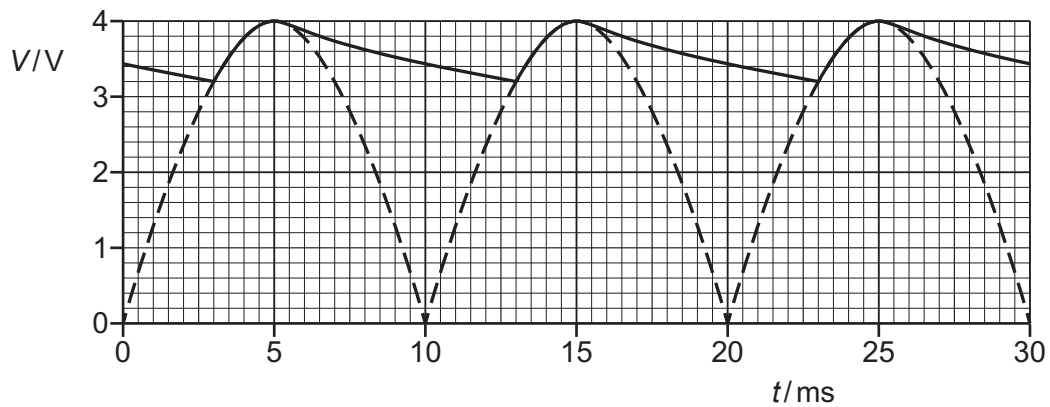


Fig. 4.3

Determine the time constant, in ms, of the smoothing circuit.

time constant = ms [3]

(d) A sinusoidal a.c. power supply has a maximum power of 16 W.

State the value of the mean power when the output of the power supply is:

(i) full-wave rectified

mean power = W [1]

(ii) half-wave rectified.

mean power = W [1]

- 4 An electron in a metal rod moves randomly about a mean position. When an alternating voltage is applied to the ends of the rod, the mean position can be considered to oscillate with simple harmonic motion along the axis of the rod. Fig. 4.1 shows the variation with time t of the displacement x of the mean position from a fixed point on the axis of the rod.

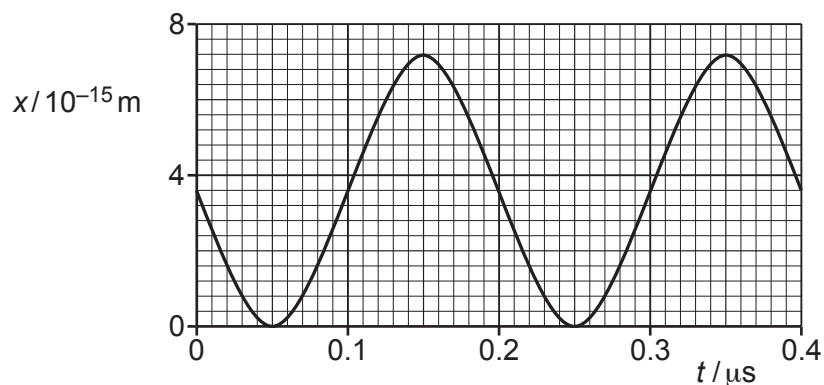


Fig. 4.1

- (a) (i) Determine the amplitude of the oscillations.

amplitude = m [1]

- (ii) Determine the angular frequency of the oscillations.

angular frequency = rad s^{-1} [1]

- (iii) Use your answers in (a)(i) and (a)(ii) to show that the maximum drift speed v_0 of the electron is $1.1 \times 10^{-7} \text{ ms}^{-1}$.

[2]

- (b) The rod has a cross-sectional area of 4.3 cm^2 and contains a number density of conduction electrons (charge carriers) of $8.5 \times 10^{28}\text{ m}^{-3}$.

All of the conduction electrons in the rod may be assumed to be oscillating in phase with, and with the same amplitude as, the oscillation shown in Fig. 4.1.

- (i) Use the information in (a)(iii) to calculate the magnitude I_0 of the maximum current in the rod.

$$I_0 = \dots\dots\dots\text{A} \quad [2]$$

- (ii) On Fig. 4.2, sketch the variation of the current I in the rod with time t between $t = 0$ and $t = 0.40\text{ }\mu\text{s}$.

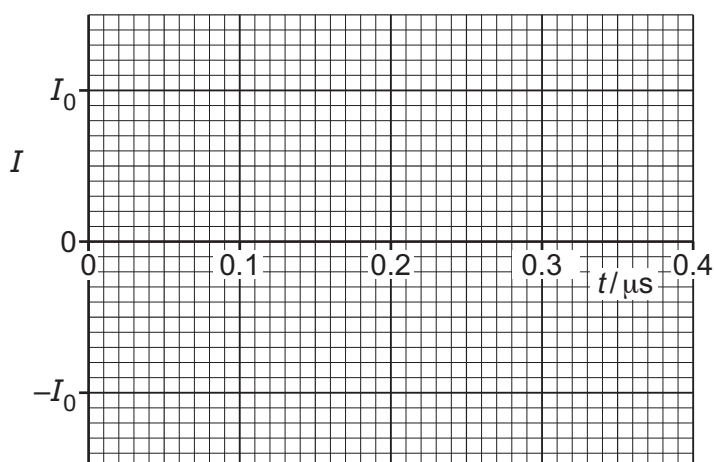


Fig. 4.2

[2]

- (iii) Use your answers in (a)(ii) and (b)(i) to determine an expression for I in terms of t , where I is in A and t is in s.

$$I = \dots\dots\dots \quad [2]$$

- (iv) Determine the root-mean-square (r.m.s.) current in the rod.

$$\text{r.m.s. current} = \dots\dots\dots\text{A} \quad [1]$$

- 7 A varying current I passes through a resistor of resistance R in the circuit shown in Fig. 7.1.

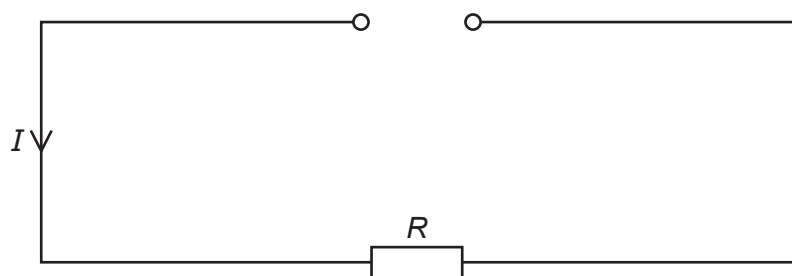


Fig. 7.1

Fig. 7.2 shows the variation with time t of I .

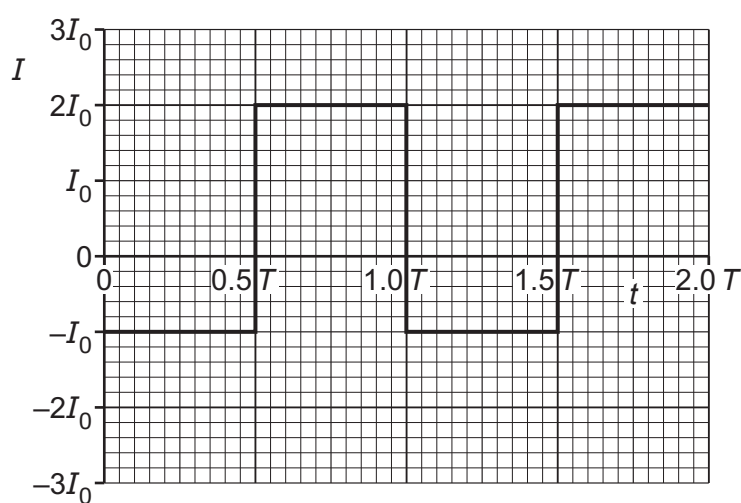


Fig. 7.2

The current has magnitude $2I_0$ when it is in the positive direction and I_0 when it is in the negative direction. The period of the variation of the current is T .

- (a) Determine expressions, in terms of I_0 and R , for the power P dissipated in the resistor for the times when:

- (i) the current is in the negative direction

$$P = \dots\dots\dots [1]$$

- (ii) the current is in the positive direction.

$$P = \dots\dots\dots [1]$$

- (b) On Fig. 7.3, sketch the variation of P with t between $t = 0$ and $t = 2.0T$. Label the power axis with an appropriate scale.

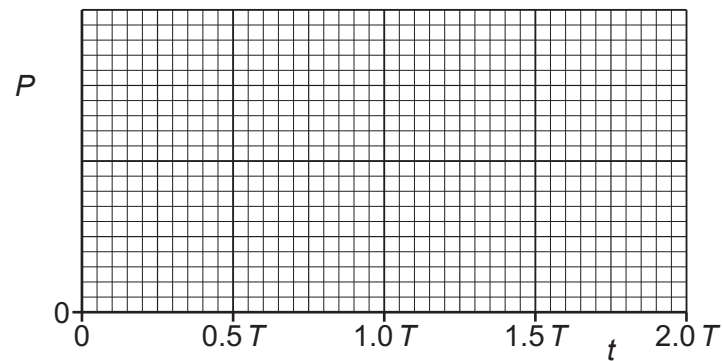


Fig. 7.3

[3]

- (c) Use your answer in (b) to determine an expression, in terms of I_0 and R , for:

- (i) the mean power $\langle P \rangle$ in the resistor

$$\langle P \rangle = \dots\dots\dots [1]$$

- (ii) the root-mean-square (r.m.s.) current $I_{\text{r.m.s.}}$ in the resistor.

$$I_{\text{r.m.s.}} = \dots\dots\dots [2]$$

(ii) Complete Fig. 7.1 by drawing the three missing diodes, correctly connected. [2]

- 7 Four diodes are used in a bridge rectifier circuit to produce rectification of a sinusoidal a.c. input voltage V_{IN} .
Fig. 7.1 shows part of the circuit, but three of the diodes are missing.

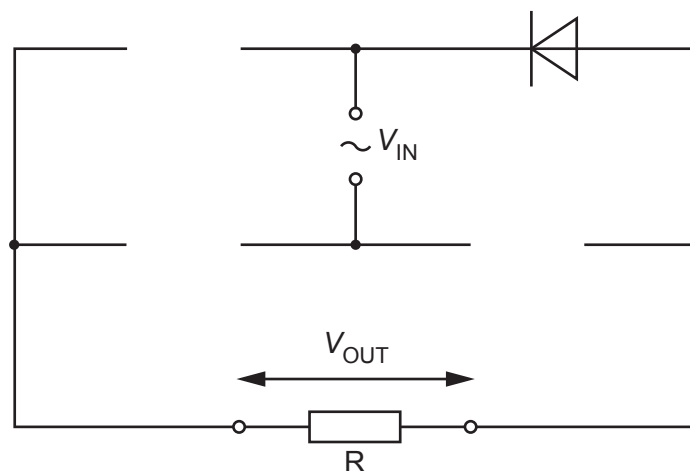


Fig. 7.1

The p.d. across the load resistor R is the output p.d. V_{OUT} of the bridge rectifier.

- (a) (i) State the name of the type of rectification produced by a bridge rectifier.

..... [1]

- (iii) On Fig. 7.1, draw an arrow to indicate the direction of the current in resistor R . [1]

- (b) V_{IN} has amplitude V_0 and period T . Fig. 7.2 shows the variation with time t of V_{IN} .

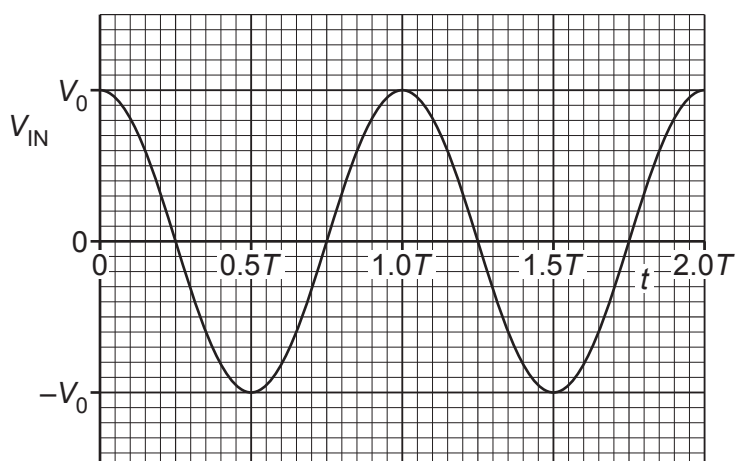


Fig. 7.2

- (i) On Fig. 7.3, sketch the variation of V_{OUT} with t between $t = 0$ and $t = 2.0T$.

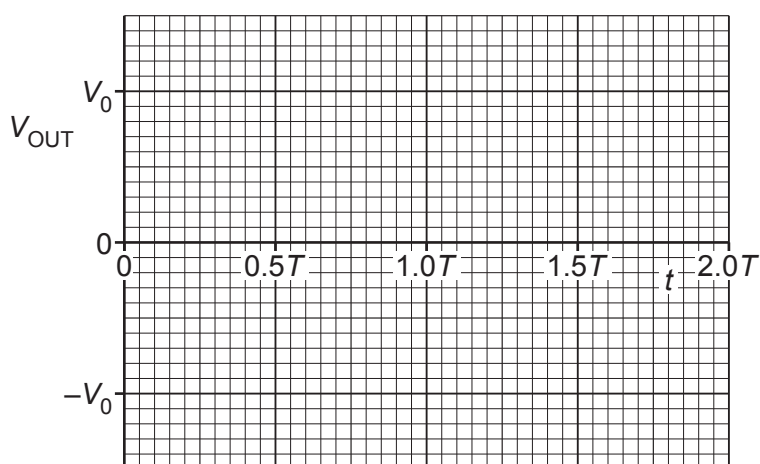


Fig. 7.3

[3]

- (ii) The power dissipated in the resistor is P .

On Fig. 7.4, sketch the variation of P with t between $t = 0$ and $t = 2.0T$.

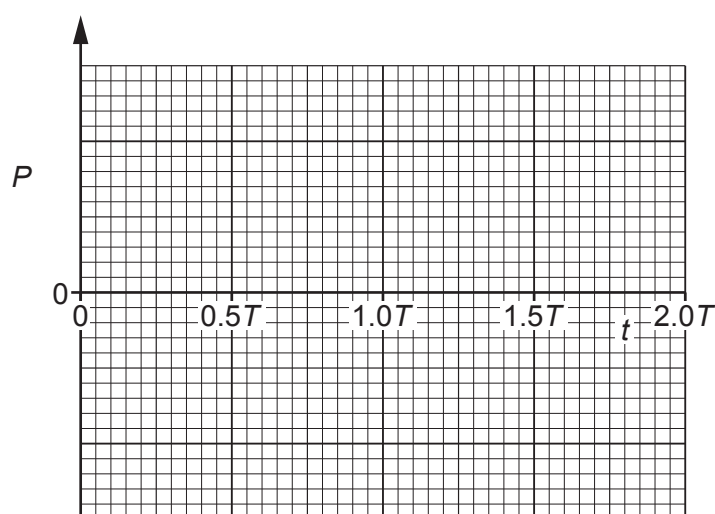


Fig. 7.4

[2]

- (iii) Suggest, with a reason, how the root-mean-square (r.m.s.) value of V_{OUT} compares with the r.m.s. value of V_{IN} .

.....
 [1]

5 Part of an electric circuit is shown in Fig. 5.1.

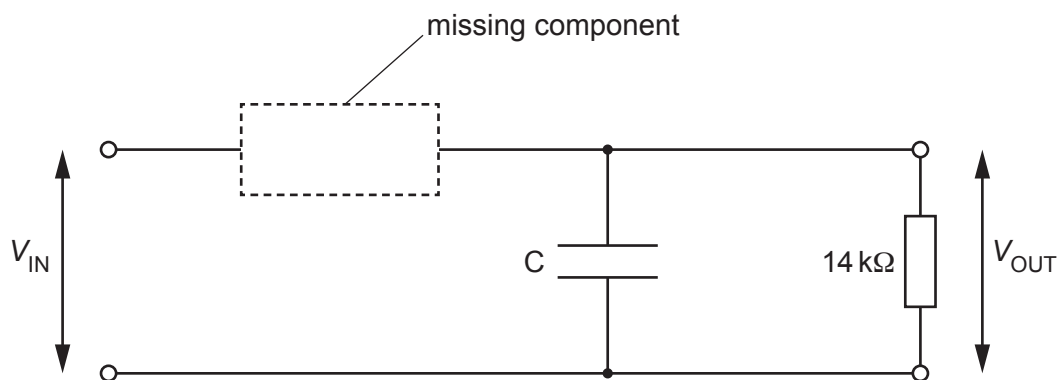


Fig. 5.1

The circuit is used to produce half-wave rectification of an alternating voltage of potential difference (p.d.) V_{IN} .

The output p.d. across the $14\text{ k}\Omega$ resistor is V_{OUT} .

(a) (i) A component is missing from the circuit of Fig. 5.1.

Complete the circuit diagram in Fig. 5.1 by adding the circuit symbol for the missing component, correctly connected. [1]

(ii) A capacitor C is shown in the circuit of Fig. 5.1.

State the effect on V_{OUT} of including the capacitor in the circuit.

..... [1]

(b) Fig. 5.2 shows the variation with time t of V_{IN} .

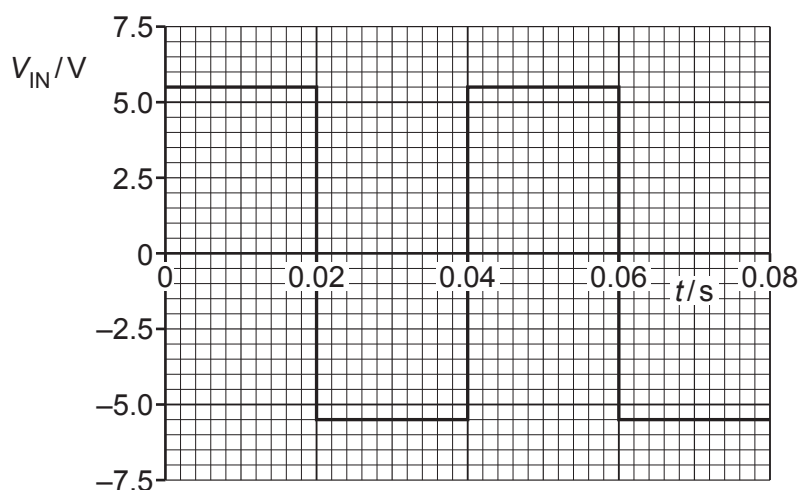


Fig. 5.2

Fig. 5.3 shows the variation with t of V_{OUT} .

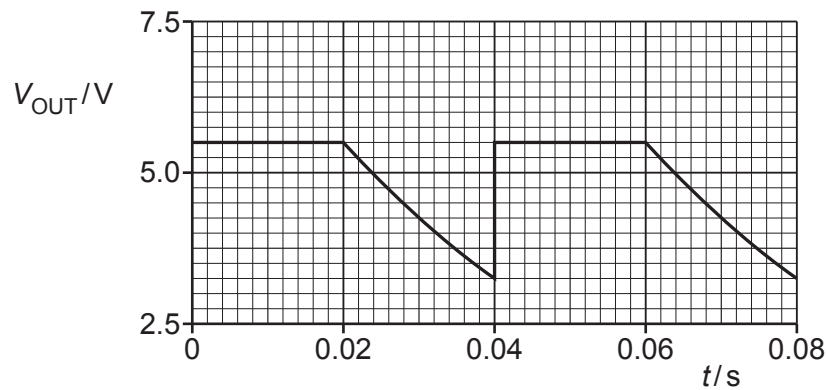


Fig. 5.3

- (i) Determine the frequency of V_{IN} .

frequency = Hz [1]

- (ii) Show that the time constant τ for the discharge of the capacitor through the resistor is 0.038 s.

[2]

- (iii) Calculate the capacitance of C. Give a unit with your answer.

capacitance = unit [2]

- (c) The circuit of Fig. 5.1 is modified so that it produces full-wave rectification of an input voltage.

Suggest, with a reason, how V_{OUT} now varies with time when V_{IN} is as shown in Fig. 5.2.

.....

 [2]

- 7 (a) A sinusoidal alternating voltage has a root-mean-square (r.m.s.) potential difference (p.d.) of 4.2 V and a frequency of 50 kHz.

- (i) The alternating voltage is applied across a resistor of resistance $760\ \Omega$.

By considering the peak voltage, show that the maximum power dissipated by the resistor is 46 mW.

[2]

- (ii) On Fig. 7.1, draw a smooth curve to show how the power P dissipated in the resistor varies with time t between $t = 0$ and $t = 40\ \mu\text{s}$. Assume that $P = 0$ when $t = 0$.

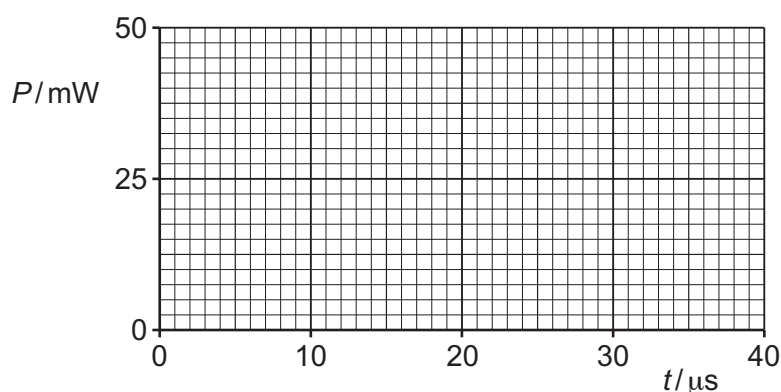


Fig. 7.1

[3]

- (iii) Use your line in (a)(ii) to explain why the mean power dissipated in the resistor is 23 mW.

.....

 [1]

- (b) The alternating voltage in (a) is now applied to a piezoelectric crystal in air.

- (i) Explain what happens to the air surrounding the crystal.

.....

 [3]

(ii) A second piezoelectric crystal is placed in the air near to the first crystal.

Explain the effect of the surrounding air in **(b)(i)** on the second crystal.

..... [1]